

Verilog RTL Coding Guideline

June 2009

Ando KI

Contents

- Purposes of coding guidelines
- Principles of coding guidelines
- Categories of coding guidelines
 - ◆ Basic coding practices
 - ◆ Coding for portability
 - ◆ Guidelines for clocks and resets
 - ◆ Coding for synthesis
 - ◆ Partitioning for synthesis

Purposes of coding guidelines

■ HDL code should be

- ◆ readable,
- ◆ modifiable, and
- ◆ reusable.

■ As a result, the HDL code is optimal result in synthesis and simulation.

Principles of coding guidelines

■ To develop RTL code that is simple and regular.

- ◆ Simple and regular structures are easier to design, code, verify, and synthesis than more complex designs.

■ General recommendations

- ◆ Use simple construct, basic types, and simple clock schemes.
- ◆ Use a consistent coding style, consistent naming conventions, and a consistent structure for processes and state machines.
- ◆ Use a regular partitioning scheme, with all module outputs registered and with modules roughly of the same size.
- ◆ Make the RTL code easy to understand, by using comments, meaningful names and constants or parameters instead of hard-coded numbers.

Categories of coding guidelines

- ▣ Basic coding practices
- ▣ Coding for portability
- ▣ Guidelines for clocks and resets
- ▣ Coding for synthesis
- ▣ Partitioning for synthesis

Basic coding practices

- ▣ Addressing basic coding practices, focusing on lexical conventions and basic RTL constructs.
- ▣ General naming conventions
- ▣ Including headers in source files
- ▣ Use comments
- ▣ Keep commands on separate lines
- ▣ Line length
- ▣ Indentation
- ▣ Do not use HDL reserved words
- ▣ Port ordering
- ▣ Port maps and generic maps
- ▣ Use functions

General naming conventions (1/2)

❏ Rule: develop a naming convention for the design, which must be documented and used consistently throughout the design.

❏ Guidelines

- ◆ Use lowercase letters for all signal names, variable names, and port names.
- ◆ Use uppercase letters for names of constants and user-defined types.
- ◆ Use meaningful names for signals, ports, functions, and parameters.
- ◆ Use short name, but descriptive names for parameters.
- ◆ Use 'clk' as the prefix for all clock signals.
- ◆ Use '_n' (or '_b') as the postfix for all active all signals.
- ◆ Use 'rst' for reset signals. If it is active low, then use 'rst_n'.
- ◆ Use a consistent ordering of bits for multi-bit buses.
- ◆ Use the same name or similar names for ports and signals that are connected.

General naming conventions (2/2)

❏ Signal name conventions

convention	Use
*_b	Active low signal (rst_b)
*_r	Output of a register (count_r)
*_a	Asynchronous signal (addr_strobe_a)
*_pn	Signal used in the nth phase (enable_p2)
*_nxt	Data before being registered into a register with the same name
*_z	Trisate internal signal
clk*	Use 'clk' as a prefix for clock signals
rst*	Use 'rst' as a prefix for reset signals

Include headers in source files

❏ Rule: include a header file at the top of every source file, including scripts.

❏ Syntax of header

- ◆ Filename
- ◆ Author
- ◆ Description of functions
- ◆ List of key features
- ◆ Date the file was created
- ◆ Modification history including date, name of modifier, and description of the change

```
/******  
 * Copyright (c) 2005 by Ando Ki.  
 * All right reserved.  
 *  
 * http://www.dynalith.com  
*****  
 * File: euclide.v  
 * Author: Ando Ki  
 * Abstract: Euclide GCD (greatest common divisor)  
 *           computes the greatest common divisor  
 *           of two non-negative integers.  
 * Date: 2005.09.30  
 * Revision history:  
 *   2005.10.01 Ando Ki 0.2 refinement  
 *   2005.09.20 Ando Ki 0.1 original  
*****  
 */  
  
module GCD ( clk, reset, a, b, valid, c, done);  
    ...  
    ...  
endmodule
```

Use comments

❏ Rule: use comments appropriately to explain all processes, functions, and declarations of types and subtypes.

❏ Guidelines

- ◆ Use comments to explain ports, signals, and variables, or groups of signals or variables.
- ◆ Comments should be brief, concise, and explanatory.
- ◆ Comments should be placed logically, near the code that they describe.

Keep commands on separate lines

■ Rule: use a separate line for each HDL statement.

- ◆ In order to be more readable and maintainable.

Line length

■ Rule: keep the line length to 72 character or less.

Indentation

❏ Rule: use indentation to improve the readability of continued code lines and nested loops.

❏ Guideline

- ◆ Use indentation of 2 spaces.
 - ❏ Large indentation restricts line length when there are several levels of nesting.
- ◆ Avoid using tabs.
 - ❏ Differences in editors and user setups make the positioning of tabs unpredictable and can corrupt the intended indentation.

Do not use HDL reserved words

❏ Rule: do not use HDL (Verilog and VHDL) reserved words for names of any elements in RTL source files.

- ◆ Macro designs must be translatable from Verilog to VHDL and vice verse.

Port ordering

❏ Rule: declare ports in a logical order, and keep this order consistent throughout the design.

❏ Guideline

- ◆ Declare one port per line, with a comment following it.
- ◆ Declare the ports in the following order.
 - ❏ inputs
 - ❑ Clocks, resets, enables, controls, data and address
 - ❏ Outputs
 - ❑ Clocks, resets, enables, controls, data

Port maps and generic maps

❏ Guideline: always use explicit mapping for ports and generics, using named association rather than positional association.

❏ Guideline

- ◆ Leave a blank line between the input and output ports to improve readability.

```
//-----  
gcd Ugcd (  
    .clk (clk),  
    .reset(reset),  
    .A (A),  
    .B (B),  
    .valid (valid),  
    .C (C),  
    .done (done)  
);
```


Use functions

■ Guideline

- ◆ Use functions when possible, instead of repeating the same sections of code.

```
//-----  
function [`WIDTH-1:0] conv_addr;  
  input  [`WIDTH-1:0] input_addr;  
  input                offset;  
begin  
  ...  
  ...  
end  
endfunction
```

Coding for portability

- Create code that is technology-independent, compatible with various simulation tools, and easily translatable from Verilog to VHDL (or from VHDL to Verilog).
- Do not use hard-coded numeric values
- Include files
- Avoid embedding dc_shell scripts
- Use technology-independent libraries

Do not use hard-coded numeric values

Guideline

- ◆ Do not use hard-coded numeric values.
 - Use constants instead of hard-coded values

```
//-----  
wire [7:0] my_in_bus;  
reg [15:0] my_reg;
```



```
`define MY_BUS_SIZE 8  
`define MY_REG_SIZE 16  
parameter MY_BUS_SIZE = `MY_BUS_SIZE  
parameter MY_REG_SIZE = `MY_REG_SIZE  
//-----  
wire [MY_BUS_SIZE-1:0] my_in_bus;  
reg [MY_REG_SIZE-1:0] my_reg;
```

Include files

Guideline

- ◆ Keep the `define statements for a design in a single separate file and name the file DesignName_params.v.

Avoid embedding dc_shell scripts

Guideline

- ◆ Avoid using dc_shell script in the source code in order to portability reason.

Use technology-independent libraries

Guideline

- ◆ Use the DesignWare Foundation Library to maintain technology independence.
- ◆ Avoid instantiating gates in the design
 - ✿ Gate-level design is hard to read, and thus difficult to maintain and reuse.
 - ✿ Technology-specific gates make the design non-portable.
- ◆ Use GTECH library, if gate must be used.
 - ✿ GTECH library (Synopsys generic technology library – one of technology-independent library) contains technology independent logical components
 - AND, OR, NOR, flip-flops, ..

DesignWare Foundation Library includes the followings

- ◆ Adders, multipliers, comparators, incrementers, and decrementers.
- ◆ Sine, cos, modulus, divide, square root, arithmetic and barrel shifters.

DesignWare library provides improved timing performance over the equivalent internal Design Compiler architectures.

- ◆ DesignWare library components are all high-performance designs that are portable across processes.

Guidelines for clocks and resets


- ❑ A simple clocking structure is easier to understand, analyze, and maintain.
- ❑ In addition to this, a simple clocking structure helps to produce better synthesis results.
- ❑ Avoid mixed clock edges
- ❑ Avoid clock buffers
- ❑ Avoid gated clocks
- ❑ Avoid internally generated clocks
- ❑ Gated clocks and low power designs
- ❑ Avoid internally generated resets

Copyright © 2014 by Ando Ki

Verilog coding guideline (23)

Ideal clocking structure

 - ❑ The preferred clocking structure is
 - ◆ A single global clock, and
 - ◆ Positive edge-triggered flops as the only sequential devices.




Copyright © 2014 by Ando Ki

Verilog coding guideline (24)

Avoid mixed clock edges (1/2)

Guideline

 - ◆ Avoid using both positive-edge and negative-edge triggered flip-flops.



Bad example: mixed clock edges

- Mixed clock edges can be used for very aggressive timing goals, such as DDR (double data rate).


The cares must be taken.

- ◆ The duty cycle is critical, since it is a critical issue in timing analysis in addition to frequency.
- ◆ Scan-based testing requires separate handling of positive and negative triggered flops.

Avoid mixed clock edges (1/2)

- Rule: be sure to model the worst case duty cycle of the clock accurately in synthesis and timing analysis, if both edges are necessary.

 
- ◆ 50% duty cycle is optimistic
 - Giving signals half the clock cycle to propagate from one register to the next.



- Rule: be sure to document the assumed duty cycle

Guideline

 - ◆ It may be useful to separate positive & negative edge flip-flops into different modules.



Better example: separated modules

Avoid clock buffers

Guideline

- ◆ Avoid hand instantiating clock buffers in RTL code.
 - ❏ Clock buffers are morally inserted after synthesis as part of the physical design.
 - ❏ In synthesizable RTL code, clock nets are normally considered ideal nets, with no delays.
 - ❏ During place and route, the clock tree insertion tool inserts the appropriate structure for creating as close to an ideal, balanced clock distribution network as possible.

Copyright © 2014 by Ando Ki

Verilog coding guideline (27)



Avoid gated clocks

Guideline

- ◆ Avoid coding gated clocks in RTL, since clock gating circuits tend to be technology specific and timing dependent.

Improper timing of a gate clock can cause

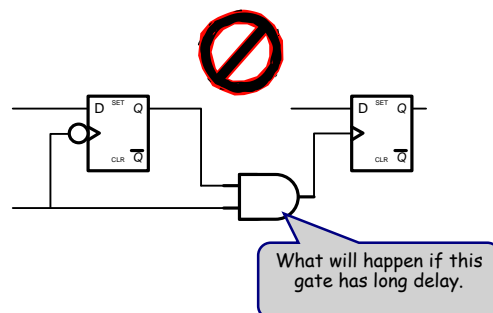 - ◆ A false clock or glitch,
- ◆ Set-up and hold time violation.




Copyright © 2014 by Ando Ki

Verilog coding guideline (28)

Avoid internally generated clocks

Guideline

 - ◆ Avoid using internally generated clocks.
- ◆ It cause limited testability since logic driven by the internally generated clock cannot be made part of a scan chain.



Copyright © 2014 by Ando Ki


Verilog coding guideline (29)

Gated clocks and low power designs

Guideline

- ◆ Keep the clock and/or reset generation circuitry (for a gate clock, an internally generated clock or reset) as a separate module at the top level.
- ◆ Partition the design so that all the logic in a single module uses a single clock and a single reset.

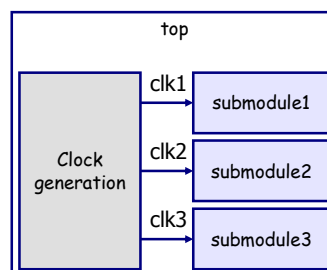- A gated clock should never occur within a macro.
- Isolating clock and reset generation logic in a separate module enables to use the standard timing analysis and scan insertion techniques.



Copyright © 2014 by Ando Ki

Verilog coding guideline (30)

Avoid internally generated resets

Guideline

- ◆ Avoid internally generated, conditional reset if possible.
 - ❖ Generally, all the registers in the macro should be reset at the same time.
- ◆ If a conditional reset is required, create a separate signal for the reset signal, and isolate the conditional reset logic in a separate module.

```
module poor_style (clk, rst, a, b);
  input clk;
  input rst;
  input a, b;
  reg [7:0] my_reg;
  always @ (posedge clk or rst or a or b) begin
    if ((rst or a or b) == 1) my_reg = 8'b0;
    else begin
      ...
    end
  end
endmodule
```



```
module better_style (rst_out, rst_in, a, b);
  output rst_out;
  input rst_in;
  input a, b;
  wire rst_out = rst_in | a | b;
endmodule

module better_style (clk, rst);
  input clk, rst;
  reg [7:0] my_reg;
  always @ (posedge clk or rst) begin
    if (rst == 1) my_reg = 8'b0;
    else begin
      ...
    end
  end
endmodule
```

Copyright © 2014 by Ando Ki

Verilog coding guideline (31)

Coding for synthesis

❑ In order to create code that achieves the best compile times and synthesis results.

- ◆ Testability
 - ◆ Performance
 - ◆ Simplification of static timing analysis
 - ◆ Gate-level circuit behavior that matches that of the original RTL code
- ❑ Infer registers
 - ❑ Avoid latches
 - ❑ Avoid combinational feedback
 - ❑ Specify complete sensitivity lists
 - ❑ Blocking and non-blocking assignments
 - ❑ Case statements v.s. if-then-else statements
 - ❑ Coding state machines

Copyright © 2014 by Ando Ki

Verilog coding guideline (32)

Infer registers

Guideline

- ◆ Registers (flip-flops) are the preferred mechanism for sequential logic.
- ◆ Use designer's reset signal to initialize registered signals.
 - Do not use initial statement to initialize the signal, since it is not synthesizable construct.
 - These can cause mismatches between pre-synthesis and post-synthesis simulation.

```
// process with synchronous reset
always @ (posedge clk)
begin : INFER_REG_PROC
    if (rst == 1'b1) begin
        ... something ...
    end else begin
        ... something else ...
    end
end // INFER_REG_PROC
```


```
// process with asynchronous reset
always @ (posedge clk or negedge rst_n)
begin : INFER_REG_PROC
    if (rst_n == 1'b0) begin
        ... reset behavior ...
    end else begin
        ... normal behavior ...
    end
end // INFER_REG_PROC
```

Avoid latches (1/2)

Rule: avoid using any latches


Latch

 - ◆ When CLK = 1, latch is *transparent*
 - D flows through to Q like a buffer
- ◆ When CLK = 0, the latch is *opaque*
 - Q holds its old value independent of D
- ◆ a.k.a. *transparent latch* or *level-sensitive latch*



Flip-flop

 - ◆ When CLK rises, D is copied to Q
- ◆ At all other times, Q holds its value
- ◆ a.k.a. *positive edge-triggered flip-flop*, *master-slave flip-flop*



Avoid latches (2/2)


What makes unintended latch inference.

- Missing assignment
- Missing condition

How to avoid the unintended latch inference.

- Avoid latch by fully assigning outputs for all input conditions using else and default.
 
```
// process causes latch inference
always @ (a or en) if (en==1'b1) q = a;
// its semantics imply that q must hold
// its old value when en is low.
```




```
// process without latch inference
always @ (a or en) if (en==1'b1) q = a; else q = 1'b0;
```



Avoid combinational feedback

Guideline

- Avoid combinational feedback.

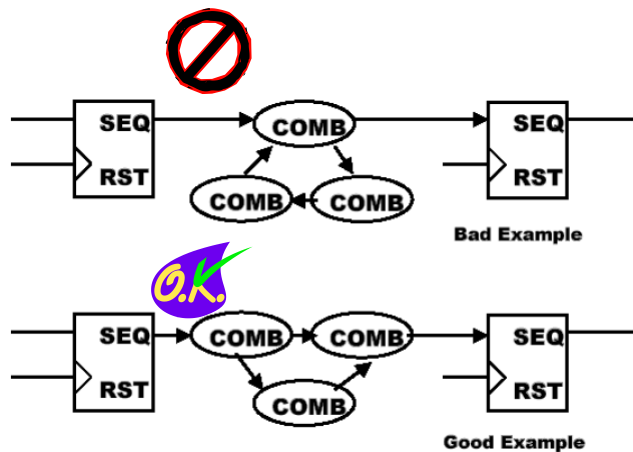

Specify complete sensitivity lists (1/2)

❏ Rule: include a complete sensitivity list in each of always blocks.


- ◆ If not, the behavior of the pre-synthesis design may differ from that of the post-synthesis netlist.

❏ Guideline


- ◆ For combinational blocks (blocks with no registers or latches), the sensitivity list must include every signal that is read by the process.
- ◆ For sequential blocks, the sensitivity list must include the clock signal that is read by the process.
- ◆ Make sure the sensitivity lists contains only necessary signals.
 - ❏ Adding unnecessary signals to the sensitivity list slows down simulation.

Specify complete sensitivity lists (2/2)
 
```
// process with incomplete sensitivity list
always @ (a) c = a or b;
```



Pre-synthesis simulation waveform

 


Post-synthesis simulation waveform



Synthesis netlist
 
```
// process with complete sensitivity list
always @ (a or b) c = a or b;
```





Blocking & non-blocking assignments (1/3)

- Blocking assignments execute in sequential order,
- While non-blocking assignments execute concurrently.
- Rule: use non-blocking assignment (\leq) in always blocks.

Blocking & non-blocking assignments (2/3)

Blocking assignments
  
```
always @
(posedge clk)
begin
  a = y;
  b = a;
end
```





Blocking & non-blocking assignments (2/3)

Non-blocking assignments

```
always @
(posedge clk)
begin
  a <= y;
  b <= a;
end
```
  
```
always @
(posedge clk)
begin
  b = a;
  a = y;
end
```




Case statements v.s. if-then-else statements (1/2)


- ❏ A case statement infers a single-level multiplexer,
- ❏ While an if-then-else statement infers a priority-encoded, cascaded combination of multiplexers.
- ❏ Guideline
 - ◆ The multiplexer is a faster circuit.

Case statements v.s. if-then-else statements (2/2)

 
```
always @ (sel or a or b or c or d)
if (sel == 2'b00) out = a;
else if (sel == 2'b01) out = b;
else if (sel == 2'b10) out = c;
else out = d;
```


 
```
always @ (sel or a or b or c or d)
case (sel)
2'b00: out = a;
2'b01: out = b;
2'b10: out = c;
default: out = d;
endcase
```



```
assign c = (s) ? b : a;
```

 


Copyright © 2014 by Ando Ki

Verilog coding guideline (43)

Coding state machines

Guideline

 - ◆ Separate the state machine HDL description into two processes, one for the combinational logic and one for the sequential logic.
- ◆ Use `define statements to define the state vector.
- ◆ Keep FSM logic and non-FSM logic in separate modules.
- ◆ Assign a default state for the state machine.



```
.....
reg [1:0] state, next_state; // FSM state
//-----
parameter IDLE   = 2'h0;
parameter FOUND  = 2'h1;
parameter MODULUS = 2'h2;
parameter DONE   = 2'h3;
//-----
always @ (state)
case (state)
IDLE: begin
...
next_state <= FOUND;
end // IDLE
FOUND: begin
...
next_state <= DONE;
end // FOUND
endcase
always @ (posedge clk or negedge rst_b)
if (rst_b == 1'b0) state <= IDLE;
else state <= next_state;
endmodule
```


Copyright © 2014 by Ando Ki

Verilog coding guideline (44)

State machine


Mealy state machine

 - ◆ The output logic is always a function of the current state (state vector) and the inputs.



Moore state machine

 - ◆ The output logic is only a function of the current state, i.e. inputs are not included.



Copyright © 2014 by Ando Ki

Verilog coding guideline (45)

Partitioning for synthesis

- Register all outputs
- Locate related combinational logic in a single module
- Separate module that have different design goals
- Asynchronous logic
- Arithmetic operations: merging resources


Copyright © 2014 by Ando Ki

Verilog coding guideline (46)

Register all outputs

Guideline

 - ◆ For each block of a hierarchical design, register all output signals from the block.
- ❖ Registering the output signals from each block simplifies the synthesis process because it makes output drive strengths and input delays predictable.




Copyright © 2014 by Ando Ki

Verilog coding guideline (47)


Locate related combinational logic in a single module

Guideline

 - ◆ Keep related combinational logic together in the same module.
- ❖ Synthesizer has more flexibility in optimizing a design when related combinational logic is located in the same module.
- ❖ Keep related combinational logic in the same module also eases time budgeting and allows for faster simulation.



Poor example

 

Better example


Copyright © 2014 by Ando Ki

Verilog coding guideline (48)

Separate modules that have different design goals

Guideline

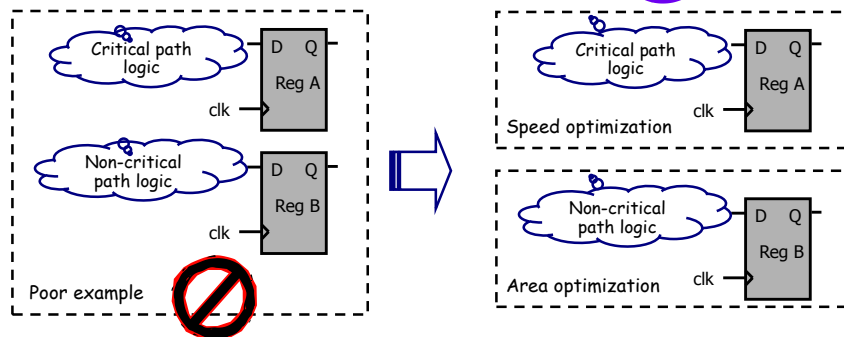- ◆ Keep critical path logic in a separate module from non-critical path logic.
- ✿ Synthesizer can optimize the critical path logic for speed, while optimizing the non-critical path logic for area.



Copyright © 2014 by Ando Ki

Verilog coding guideline (49)

Avoid asynchronous logic

Guideline

- ◆ Avoid asynchronous logic.
- ◆ If asynchronous logic is required, partition the asynchronous logic in a separate module from the synchronous logic.
- ◆ Isolating the asynchronous logic in a separate module makes code inspection much easier.
- ◆ Asynchronous logic need to be reviewed carefully to verify its functionality and timing.


Copyright © 2014 by Ando Ki

Verilog coding guideline (50)

Avoid point-to-point exceptions

Guideline

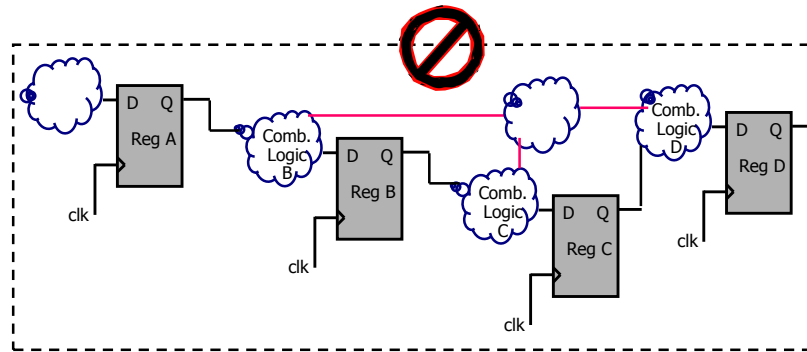- ◆ Avoid multi-cycle paths
 - ❏ Multi-cycle path is more difficult to analyze correctly.
- ◆ If needed, keep point-to-point exceptions within a single module.




Copyright © 2014 by Ando Ki

Verilog coding guideline (51)

Avoid glue logic at the top level

Guideline

 
- ◆ Do not instantiate gate-level logic at the top level of the design hierarchy.
 - ❏ Let design hierarchy contain gates only at leaf levels of the hierarchy tree.



Copyright © 2014 by Ando Ki


Verilog coding guideline (52)

Coding

 

```
wire sig_in_a;
wire sig_in_b;
wire sig_out_c;
wire sig_out_d = sig_in_a & sig_in_b;
assign sig_out_c = sig_in_a | sig_in_b;
```

 
Combinational logic inference by continuous assignment
(not wire and assign)



```
wire sig_in_a;
wire sig_in_b;
reg sig_out_c;
reg sig_out_d;

always @ (posedge clk) begin
    sig_out_d <= sig_in_a & sig_in_b;
    sig_out_c <= sig_in_a | sig_in_b;
end
```

 Register or Flip-Flop inference by always block
(note "posedge clk")




```
wire sig_in_a;
wire sig_in_b;
reg sig_out_c;
reg sig_out_d;

always @ ( * ) begin
    sig_out_d <= sig_in_a & sig_in_b;
    sig_out_c <= sig_in_a | sig_in_b;
end
```

Combinational logic inference by always block
(note event list or sensitivity list)

Coding

 

```
wire sig_in_a;
wire sig_in_b;
wire sig_out_c;
wire sig_out_d;
reg sig_reg_x;
reg sig_reg_y;

always @ (posedge clk) begin
    sig_reg_x <= sig_in_a & sig_in_b;
    sig_reg_y <= sig_in_a | sig_in_b;
end

assign sig_out_c = sig_reg_x & sig_reg_y;
assign sig_out_d = sig_reg_x | sig_reg_y;
```

Reading

■ M. Keating and P. Bricaud, Reuse Methodology Manual, Chapter 5 RTL Coding Guidelines, KAP, 1999.