

Clock Domain Crossing


2014 - 2020

Ando Ki, Ph.D.
(adki@future-ds.com)


Agenda

- ❑ Clock frequency and phase
- ❑ Setup and hold time
- ❑ Slack
- ❑ Metastability
- ❑ Clock domain crossing

Clock frequency and phase

 


Setup and hold time

 

Setup time: The time data must remain stable before clock transitions on a flip-flop.


Hold time: The length of time of a flip-flop's input data must remain stable after the each clock transition.

 Violating the setup and hold time will create a metastable state, which is a condition giving a random data.



		min	typ	max
Setup		0ns		
Hold		0.2ns		
propagation	PLH	2ns	6ns	10ns
	PHL	2ns	6ns	10ns

Slack

 


❑ Setup slack = (data required time) – (data arrival time)

❑ Hold slack = (data arrival time) – (data required time)


- ◆ (data required time for setup) = (clock period) – (setup) → signal should be valid before rising edge of clock
- ◆ (data required time for hold) = (clock period) + (hold)

❑ Negative setup slack implies that design doesn't achieve the constrained frequency and timing. This is called as setup violation

Good: Positive Slack

 

Bad: Negative Slack


 


Copyright © 2014 by Ando Ki

Clock Domain Crossing (5)

Metastability

  
❑ Whenever the input signal D does not meet the Tsu (Setup) and Th (Hold) of the given D flip-flop, metastability occurs.



Copyright © 2014 by Ando Ki

Clock Domain Crossing (6)


CDC: Clock-Domain Crossing

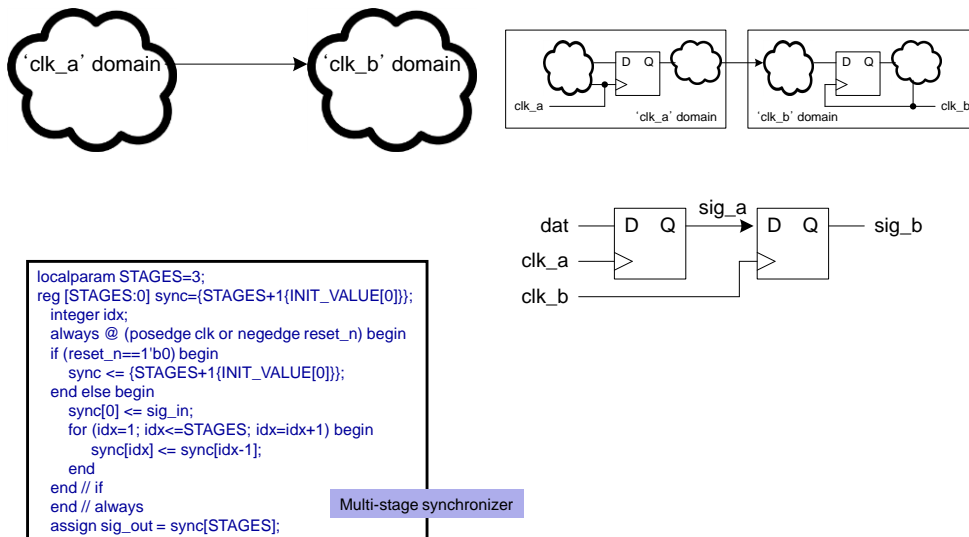

Copyright © 2014 by Ando Ki

Clock Domain Crossing (7)

CDC: Meta-stability

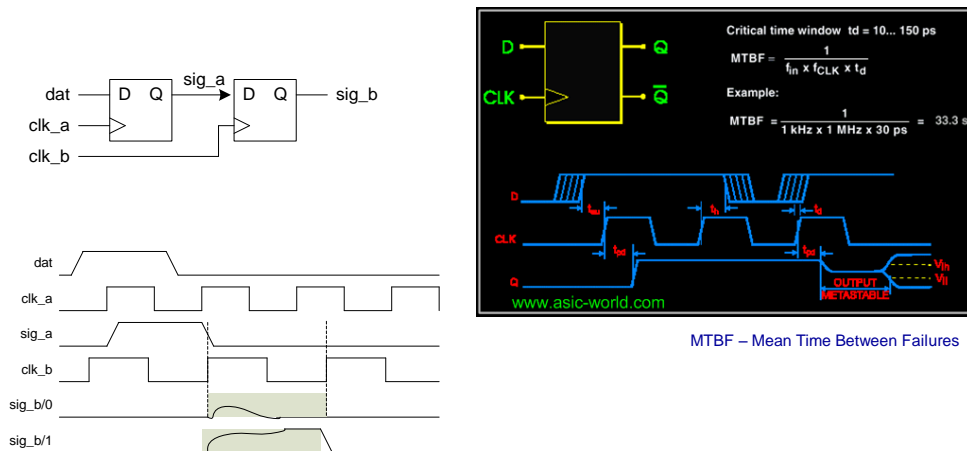


'sig_b' can be settle down to '0' or '1' depending on situation (fan-out, temperature, ...).

Copyright © 2014 by Ando Ki


Clock Domain Crossing (8)

CDC: Multi-flip-flop synchronization

 

Multi-stage synchronizer

```
localparam STAGES=3;
reg [STAGES:0] sync={STAGES+1{INIT_VALUE[0]}};
integer idx;
always @ (posedge clk or negedge reset_n) begin
    if (reset_n==1'b0) begin
        sync <= {STAGES+1{INIT_VALUE[0]}};
    end else begin
        sync[0] <= sig_in;
        for (idx=1; idx<=STAGES; idx=idx+1) begin
            sync[idx] <= sync[idx-1];
        end
    end // if
end // always
assign sig_out = sync[STAGES];
```

 


Copyright © 2014 by Ando Ki

Clock Domain Crossing (9)



CDC: data loss problem

 ■ Data can be lost with fast-to-slow clock domain




■ Solutions

  - ◆ Edge detection
- ◆ Feedback or handshake



Copyright © 2014 by Ando Ki

Clock Domain Crossing (10)

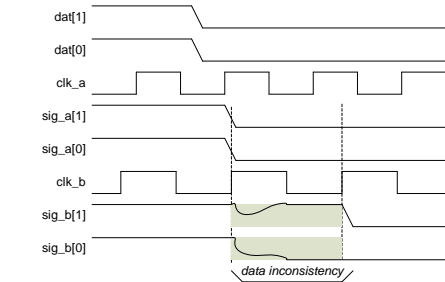 Solutions

- Copyright © 2014 by Ando Ki Clock Domain Crossing (11)

