

Verilog RTL Coding Guideline for Synthesis and Simulation

May 2014

Ando KI

Contents

■ Coding guideline for synthesis

- ◆ What for
- ◆ Terminologies
- ◆ Latch and flip-flop
- ◆ Modeling HW elements
 - Modeling combinational logic
 - Modeling edge-sensitive sequential logic
 - Modeling level-sensitive storage devices
 - Modeling tree-state drivers
 - Modeling read-only memories (ROM)
 - Modeling random access memories (RAM)

■ Coding guideline for synthesis & simulation

- ◆ Blocking and non-blocking
- ◆ Race problem
- ◆ Use parentheses
- ◆ Resource sharing
- ◆ Pre-schedule RTL
- ◆ Full case for if statement
- ◆ Full/parallel case for case statement
- ◆ Pseudo comment for full case
- ◆ Pseudo comment for parallel case
- ◆ Casex
- ◆ Casez

What for

- ❏ Define a set of modeling rules for writing Verilog HDL description for synthesis
- ❏ Define how the semantics of Verilog HDL are used
- ❏ Describe the syntax of the language with reference to what shall be supported and what shall not be supported for interoperability
- ❏ Enhance the portability of Verilog-HDL-based design across synthesis tools conforming to this standard
- ❏ Minimize the potential for functional mismatch that may occur between the RTL model and the synthesized netlist

Terminologies (1/2)

- ❏ Synchronous & asynchronous
 - ◆ Synchronous: Data that changes only on a clock edge
 - ◆ Asynchronous: Data that changes value independent of the clock edge
- ❏ Edge-sensitive & level-sensitive storage device
 - ◆ Edge-sensitive storage device: Any device mapped to by a synthesis tool that is edge-sensitive to a clock, e.g., a flip-flop.
 - ◆ Level-sensitive storage device: Any device mapped to by a synthesis tool that is level-sensitive to a clock, e.g., a latch.
- ❏ Combinational & sequential logic
 - ◆ Combinational logic: Logic that does not have any storage device, either edge-sensitive or level-sensitive.
 - ◆ Sequential logic: Logic that includes any kind of storage device, either level-sensitive or edge-sensitive.

Terminologies (2/2)

❏ Instantiation & inference

- ◆ Instantiation: explicitly select a technology-specific element in the target library.
- ◆ Inference: direct the HDL Compiler to infer latches or flip-flops or other resource blocks from your Verilog or VHDL description.


❏ Technology-independent & technology-dependent

- ◆ Keeping the pre-synthesis design source code technology-independent allows you to re-target to other technologies at a later time, with a minimum of re-design effort.
- ◆ Technology-dependent design uses dedicated functions or design techniques optimized for speed or area
 - The designer may require detailed understanding on device architectures

Latch and flip-flop


❏ Latch

 - ◆ When $en = 1$, latch is *transparent*
 - D flows through to Q like a buffer
- ◆ When $en = 0$, the latch is *opaque*
 - Q holds its old value independent of D
- ◆ a.k.a. *transparent latch* or *level-sensitive latch*



❏ Flip-flop

 - ◆ When CLK rises, D is copied to Q
- ◆ At all other times, Q holds its value
- ◆ a.k.a. *positive edge-triggered flip-flop*, *master-slave flip-flop*



Modeling hardware elements

- ❑ Modeling combinational logic
- ❑ Modeling edge-sensitive sequential logic
- ❑ Modeling level-sensitive storage devices
- ❑ Modeling tri-state drivers
- ❑ Modeling read-only memories (ROM)
- ❑ Modeling random access memories (RAM)

Copyright © 2014 by Ando Ki

Verilog coding guideline (7)

Modeling combinational logic

- ❑ Continuous assignment
- ❑ Net declaration assignment
- ❑ Always statement
 - ◆ Event list shall not contain an edge event (posedge or negedge)
 - ◆ Event list must include all the variables read in the always statement
 - If not, mismatch can occur between simulation and synthesized logic.
 - ◆ Shall not use both a blocking assignment (=) and a non-blocking assignment (<=) in the same always statement

```
wire my_signal = A + B;
```

```
wire your_signal;  
assign your_signal = A + B;
```

```
always @ (in1 or in2) out = in1 + in2;
```

```
always @ (*) begin  
    tmp1 = a & b;  
    tmp2 = c & d;  
    z     = tmp1 | tmp2;  
end  
// implicit event list expression yields comb. logic
```

```
always @ (posedge a or b) ... ..  
// not supported; does not model comb. Logic
```

```
always @ (in) if (ena) out = in;  
                else out = in2;  
// should be always @ (in or ena) ...
```

```
always @ (in1 or in2 or ena) if (ena) out = in1;  
                                else out <= in2;  
// don't mix = and <= in an always statement
```

Copyright © 2014 by Ando Ki

Verilog coding guideline (8)

Modeling edge-sensitive seq. logic

- Sequential logic shall be modeled using an always statement that has one or more edge event in the event list.

```
// positive edge
always @ (posedge <clock_name>) ... ..


// negative edge
always @ (negedge <clock_name>) ... ..
```

Modeling edge-sensitive storage devices

- An edge-sensitive storage shall not use multiple event lists
- Nonblocking procedural assignment should be used
- Multiple event lists are not supported within an always statement

```
reg out;
...
always @ (posedge clock) out <= in;
// out: pos-edge triggered storage

 reg [3:0] out;
always @ (negedge clock) out <= in;
// out: neg-edge triggered storage with 4 elements
```



```
always @ (posedge clock) begin
    out <= 0;
    @ (posedge clock);
    out <= 1;
end
// not legal: multiple-edge event list
```



Edge-sensitive with synchronous set/reset

- ❏ An edge-sensitive storage device with a synchronous set/reset is modeled using an always statement whose event list only contains edge events representing the clock.

```
reg out;
...
always (posedge clock) if (reset) out <= 1'b0;
                        else out <= in;
// synchronous reset

always @ (posedge clock) if (set) out <= 1'b1;
                        else out <= in;
// synchronous set
```



```
always @ (posedge clock or reset) begin
    if (reset) out <= 1'b0;
    else out <= in;
end
// do not mix edge and level sensitive event
```



Edge-sensitive with asynchronous set/reset (1/2)

- ❏ An edge-sensitive storage device with an asynchronous set/reset is modeled using an always statement whose event list contains edge events representing the clock and asynchronous control variables.
- ❏ Level-sensitive events shall not be allowed in the event list of an edge-sensitive storage device model.
- ❏ The first if and optional else if statements model asynchronous control and a final else statement specifies the synchronous logic portion.

```
// generic form
always @ (posedge <condA> or negedge <condB>
        or negedge <condC> or ...
        or posedge <clock>)
if (condA) // positive polarity
    ... // asynchronous logic
else if (~<condB>) // negative polarity
    ... // asynchronous logic
else if (~<condC>)
    ... // asynchronous logic
else if ...
else // implicit posedge <clock>
    ... // synchronous logic
```

- ◆ Any sequence of edge events can be in event list.

- ◆ The final else statement
 - ✦ If there are N edge events in the event list, the else following (N-1) if's, at the same level as the top-level if statement, determines the final else.

Edge-sensitive with asynchronous set/reset (2/2)

```
always @ (posedge clock or posedge set)
  if (set) out <= 1'b1;
  else   out <= din;
// edge-sensitive storage with asynchronous set

always @ (posedge clock or negedge reset)
  if (~reset) out <= 1'b0;
  else       out <= din;
// edge-sensitive storage with asynchronous reset

always @ (posedge clock or negedge clear)
  if (~clear) out <= 0;
  else
    if (ping)   out <= in;
    else if (pong) out <= 8'bFF;
    else       out <= din;
// synchronous logic starts after the first else
```



```
always @ (posedge clock or posedge reset)
  out <= in;
// not legal: the if statement is missing



always @ (posedge clock or negedge clear)
  if (clear) out <= 0;
  else      out <= in;
// not legal: if condition does not match the polarity
// of the edge event
```





Modeling level-sensitive storage devices

- ❑ The event list does not contain a edge events (posedge or negedge).
 - ◆ The same as the combinational logic.
- ❑ The event list of the always statement should list all variables read within the always statement.
 - ◆ The same as the combinational logic.
- ❑ There is no explicit assignment to the variable.
 - ◆ Implicitly value keeping semantics.
- ❑ Nonblocking procedural assignment should be used for variable.
- ❑ Note: it is latch inference intentionally.
  
```
always @ (en or d) if (en) q <= d;
// If en is deasserted, q will hold its value.
```



  
```
always @ (en or d)
  if (en) q <= d;
  else   q <= 'b0;
// Latch is not inferred, but a combinational logic.
// q is assigned on every execution of the always
// statement → meaning combinational logic.
```



Modeling tri-state drivers (1/3)

 
Tri-state logic shall be modeled when a variable is assigned the value z.




```
always @ (q or en)
if (!en) out <= 'bz;
else    out <= q;
// out is a three-state driver.
```

```
module ztest (test2, test1, test3, en);
input  [0:1] en;
input  [7:0] test1, test3;
output [7:0] test2;
wire   [7:0] test2;
assign test2 = (en == 2'b01) ? test1 : 8'bz;
assign test2 = (en == 2'b10) ? test3 : 8'bz;
// test2 is three-state when en is 2'b00 or 2'b11.
endmodule
```

Modeling tri-state drivers (2/3)

 
 
```
always @ (posedge clock) q <= din;
assign out = en ? q : 1'bz;
// one edge-sen. storage with a tri-state driver
```



```
always @ (posedge clock)
if (!en) out <= 1'bz;
else    out <= din;
// two edge-sen. storages. One for din, one for en,
// with a tri-state driver for din-out.
```


Modeling tri-state drivers (3/3)

❏ Z assignment shall not propagate across variable assignment.

```
module ztest;
  wire test1, test2, test3;
  input test2;
  output test3;
  assign test1 = 1'bz;
  assign test3 = test1 & test2;
  // test3 will never receive a z assignment
  // test2 always determines test3.
endmodule
```

```
always @ (in)
  begin
    tmp = 'bz;
    out = tmp;
    // out shall not be driven by three state drivers
    // because the value 'bz does not propagate
    // across the variable assignment.
  end
```

Modeling one-dimensional ROM

```
module rom_case(
  output reg [3:0] z,
  input wire [2:0] a; // Address - 8 deep memory.
  always @* // @(a)
  case (a)
    3'b000: z = 4'b1011;
    3'b001: z = 4'b0001;
    3'b100: z = 4'b0011;
    3'b110: z = 4'b0010;
    3'b111: z = 4'b1110;
    default: z = 4'b0000;
  endcase
endmodule // rom_case
// z is the ROM, and its address size is
// determined by a.
```

Modeling two-dimensional ROM

With fixed contents

With data in text file

```
module rom_2dimarray_initial (
  output wire [3:0] z,
  input wire [2:0] a; // address- 8 deep memory
  // Declare a memory rom of 8 4-bit registers.
  // The indices are 0 to 7:
  reg [3:0] rom[0:7];
  initial begin
    rom[0] = 4'b1011;
    rom[1] = 4'b0001;
    rom[2] = 4'b0011;
    rom[3] = 4'b0010;
    rom[4] = 4'b1110;
    rom[5] = 4'b0111;
    rom[6] = 4'b0101;
    rom[7] = 4'b0100;
  end
  assign z = rom[a];
endmodule
```

0				
1				
2				
3				
4				
5				
6				
7				

```
module rom_2dimarray_initial_readmem (
  output wire [3:0] z,
  input wire [2:0] a);
  // Declare a memory rom of 8 4-bit registers.
  // The indices are 0 to 7:
  reg [3:0] rom[0:7];
  initial $readmemb("rom.data", rom);
  assign z = rom[a];
endmodule
// with data in text file
```

// Example of content "rom.data" file:

```
1011 // addr=0
1000 // addr=1
0000 // addr=2
1000 // addr=3
0010 // addr=4
0101 // addr=5
1111 // addr=6
1001 // addr=7
```

Copyright © 2014 by Ando Ki

Verilog coding guideline (19)

Modeling RAM

RAM element with edge-sensitive

RAM element with level-sensitive

```
// A RAM element is an edge-sensitive storage
// element:
module ram_test(
  output wire [7:0] q,
  input wire [7:0] d,
  input wire [6:0] a,
  input wire clk, we);
  reg [7:0] mem [127:0];
  always @(posedge clk) if (we) mem[a] <= d;
  assign q = mem[a];
endmodule
```

```
// A RAM element is a level-sensitive storage
// element:
module ramlatch (
  output wire [7:0] q, // output
  input wire [7:0] d, // data input
  input wire [6:0] a, // address
  input wire we; // clock and write enable
  // Memory 128 deep, 8 wide:
  reg [7:0] mem [127:0];
  always @* if (we) mem[a] <= d;
  assign q = mem[a];
endmodule
```

Copyright © 2014 by Ando Ki

Verilog coding guideline (20)

Contents

▣ Coding guideline for synthesis & simulation

- ◆ Blocking and non-blocking
- ◆ Race problem
- ◆ Use parentheses
- ◆ Resource sharing
- ◆ Pre-schedule RTL
- ◆ Full case for if statement
- ◆ Full/parallel case for case statement
- ◆ Pseudo comment for full case
- ◆ Pseudo comment for parallel case
- ◆ Casex
- ◆ Casez


Blocking and non-blocking

▣ Blocking assignments (=) execute in sequential order.

▣ Non-blocking assignments (<=) execute concurrently.


Blocking assignments (1/2)
 
```
always @ (posedge clk) begin
  a = din;
  b = a;
end
```




Non-blocking assignments (1/2)
 
```
always @ (posedge clk) begin
  a <= din;
  b <= a;
end
```




Blocking assignments (2/2)
 
```
always @ (posedge clk) begin
  b = a;
  a = din;
end
```



Non-blocking assignments (2/2)
 
```
always @ (posedge clk) begin
  b <= a;
  a <= din;
end
```




Race condition

- ❑ Blocking assignments follow order of statements.
- ❑ Parallel procedures have no order.
- ❑ Thus, blocking assignments across parallel procedures can cause race condition.
 - ◆ The result depends on execution order, which is not explicitly determined.

```
always @(posedge clk) a = b;
always @(posedge clk) b = a;
// With Blocking both start at same time
// a could transfer to b first and b also could
// transfer to a first. The order is not fixed.
```

 
```
always @(posedge clk) a <= b;
always @(posedge clk) b <= a;
```



Use parentheses

- ❑ Use parentheses to control the structure of a complex design
- ❑ Use parentheses to guide synthesis

 
```
assign z1 = a + b + c + d;
assign z2 = (w + x) + (y + z);
// the same hardware blocks used,
// but z2 gives better delay-time characteristics than z1.
```




Resource sharing

- Operators can be shared within an always block by default.
- The resource sharing can help to save hardware resources, but may fail to make hardware smaller
 
```
always @(a or b or c or sel)
  if (sel) z = a + b;
  else    z = a + c;
// without sharing
// larger
```



 
```
always @(a or b or c or sel) begin
  if (sel) y = b;
  else    y = c;
  z = a + y;
end
// with sharing
// smaller
```




```
always @(SEL or A or B or C or D)
  if (SEL) Y = (A == B);
  else    Y = (C == D);
end
```

Without sharing, but smaller

 

With sharing, but larger

 

Copyright © 2014 by Ando Ki

Verilog coding guideline (25)

Pre-schedule RTL code

- Think if you can reduce logic from the architecture view before starting coding, pre-schedule your RTL design if possible.

[What wanted to be hardware]
assume there is A[31:0] and shiftcnt that is N
if a[31] == 0, result = {N{1'b0}, A[31], ..., A[N]}
if a[31] == 1, result = {N{1'b1}, A[31], ..., A[N]}

Be complex and requires more hardware

```
module shift (A, shiftcnt, z);
  input [31:0] A;
  input [4:0] shiftcnt;
  output [31:0] z;
  assign z = A[31] ? ((A >> shiftcnt)
    | (((32'b1 << shiftcnt) - 1)
      << (32 - shiftcnt)))
    : (A >> shiftcnt);
endmodule
```

Be simple and requires less hardware

```
module shift (A, shiftcnt, z);
  input [31:0] A;
  input [4:0] shiftcnt;
  output [31:0] z;
  assign z = {{31{A[31]}}, A} >> shiftcnt;
endmodule
```

Copyright © 2014 by Ando Ki

Verilog coding guideline (26)


Full case for if construct

■ Be called full when all possible outcomes are accounted for.

It is full case.

It is full case.


 
```
always @ (en or a or b)
  if (en) q <= a;
  else q <= b;
```



```
always @ (en or a or b) begin
  q = b;
  if (en) q = a;
end
```

It is not full case.
  
```
always @ (en or d) if (en) q <= d;
// If en is false, there may be need to preserve
// a previous value set onto the wire q.
```



Copyright © 2014 by Ando Ki


Verilog coding guideline (27)

Full/parallel case for case construct (1/2)


■ A case statement is called full if all possible outcomes are accounted for.

■ A case statement is called parallel if the stated alternatives are mutually exclusive.
 
```
module full_par (sel, a, b, c, d, out);
input [1:0] sel;
input a, b, c, d;
output out; reg out;
always @ (sel or a or b or c or d)
  case (sel)
    2'b11: out <= a;
    2'b10: out <= b;
    2'b01: out <= c;
    default: out <= d; // 2'b00
  endcase
endmodule
```


 
```
module par_not_full (sel, a, b, c, out);
input [1:0] sel;
input a, b, c;
output out; reg out;
always @ (sel or a or b or c)
  case (sel)
    2'b11: out <= a;
    2'b10: out <= b;
    2'b01: out <= c;
  endcase
endmodule
```




Copyright © 2014 by Ando Ki


Verilog coding guideline (28)

Full/parallel case for case construct (2/2)
 
```
module full_not_par (sel, a, b, c, out);
input [1:0] sel;
input      a, b, c;
output     out; reg out;
always @ (sel or a or b or c)
  case (sel)
    2'b1?: out <= a; // 2'b10, 2'b11
    2'b?1: out <= b; // 2'b01, 2'b11
    default: out <= c; // 2'b00
  endcase
endmodule
// If the case is 2'b11 occurs, the first outcome gets higher priority because it is closer to the output.
```


 
```
module not_full_not_par (sel, a, b, out);
input [1:0] sel;
input      a, b;
output     out; reg out;
always @ (sel or a or b)
  case (sel)
    2'b1?: out <= a; // 2'b10, 2'b11
    2'b?1: out <= b; // 2'b01, 2'b11
  endcase
endmodule
```



Copyright © 2014 by Ando Ki

Verilog coding guideline (29)

Pseudo-comment for full case

- ❑ The user may know that it is impossible for the missing case(s) to occur. Then, the user can use pseudo-comment for full case.

- ◆ // synopsys full_case
- ◆ (* synthesis, full_case *)

- ❑ Full_case indicates that all user-desired cases have been specified.

- ◆ Other cases never occurs.
- ◆ Let compiler think the cases left out be don't care.

- ❑ You can attach the full_case directive to tell the synthesis tool the Verilog case item expressions cover all the possible cases.

```
always @(SEL or A or B or C) begin
  case (SEL)
    3'b001 : OUT <= A;
    3'b010 : OUT <= B;
    3'b100 : OUT <= C;
  endcase
end
// Infers latches for OUT
// because not all cases are specified
// which make the logic keep its value
```

```
always @(SEL or A or B or C)
  case (SEL) //synopsys full_case
    3'b001 : OUT <= A;
    3'b010 : OUT <= B;
    3'b100 : OUT <= C;
    default: OUT <= 'b0;
  endcase
```

```
always @(SEL or A or B or C)
  case (SEL) // synopsys full_case
    3'b001 : OUT <= A;
    3'b010 : OUT <= B;
    3'b100 : OUT <= C;
  endcase
```

Copyright © 2014 by Ando Ki

Verilog coding guideline (30)

Pseudo comment for parallel case

❏ The user may know that the cases are really mutually exclusive. Then the user can use pseudo comment for parallel case.

- ◆ // synopsys parallel_cases
- ◆ (* synthesis, parallel_case *)

❏ Attach the parallel_case directive to improve the efficiency if no two case item expressions ever match the test expression at the same time.

- ◆ E.g., state of FSM – cannot be multiple state at the same time.

```
always @(SEL or A or B or C)
case (SEL)
A : OUT <= 3'b001
B : OUT <= 3'b010
C : OUT <= 3'b100
endcase
// infers priority encoder
```

```
always @(SEL or A or B or C)
case (SEL) // synopsys parallel_case
A : OUT <= 3'b001
B : OUT <= 3'b010
C : OUT <= 3'b100
endcase
// infers multiplexer
```


Casex

❏ The casex treats z or x or ? symbols in the expression or case items as don't – cares.

Casez


- The `casez` treats `z` or `?` symbols in the expression or case items as don't-cares.
 - ◆ The syntax of literal numbers allows the use of the question mark (?) in place of `z` in the `casez` statement.

Coding

 


```
wire sig_in_a;  
wire sig_in_b;  
wire sig_out_c;  
wire sig_out_d = sig_in_a & sig_in_b;  
assign sig_out_c = sig_in_a | sig_in_b;
```

 **Combinational logic inference by
continuous assignment
(not wire and assign)**



```
wire sig_in_a;  
wire sig_in_b;  
reg sig_out_c;  
reg sig_out_d;  
  
always @ (posedge clk) begin  
    sig_out_d <= sig_in_a & sig_in_b;  
    sig_out_c <= sig_in_a | sig_in_b;  
end
```

 
**Register or Flip-Flop inference by
always block
(note "posedge clk")**



```
wire sig_in_a;  
wire sig_in_b;  
reg sig_out_c;  
reg sig_out_d;  
  
always @ ( * ) begin  
    sig_out_d <= sig_in_a & sig_in_b;  
    sig_out_c <= sig_in_a | sig_in_b;  
end
```

**Combinational logic inference by
always block
(note event list or sensitivity list)**

Coding

 

```
wire sig_in_a;
wire sig_in_b;
wire sig_out_c;
wire sig_out_d;
reg sig_reg_x;
reg sig_reg_y

always @ (posedge clk) begin
    sig_reg_x <= sig_in_a & sig_in_b;
    sig_reg_y <= sig_in_a | sig_in_b;
end

assign sig_out_c = sig_reg_x & sig_reg_y;
assign sig_out_d = sig_reg_x | sig_reg_y;
```

References

- IEEE Standard for Verilog Register Transfer Level Synthesis, IEEE Std. 1364.1, IEEE Computer Society, Dec. 18, 2002.
- IEEE Standard Verilog Language Reference Manual, IEEE Std. 1364, IEEE Computer Society, 2001.