

Verilog

- Gate and Switch Level Modeling -

May 2014

Ando KI

Contents

■ Prerequisites

- ◆ Levels of abstraction
- ◆ Levels of modeling

■ Built-in gates and switches

■ Variable input/output logic gates

■ Buffers and tri-state buffers

■ MOS switches

■ Bidirectional pass switch

■ Pullup and pulldown

■ Gate delay

■ Examples

■ UDP


- ◆ Form of UDP
- ◆ UDP table
- ◆ Combinational UDP example
- ◆ Sequential UDP example

Levels of abstraction

Structural levels


◆ Switch level

 - Referring to the ability to describe the circuit as a netlist of transistor switches.



◆ Gate level

 - Referring to the ability to describe the circuit as a netlist of primitive logic gates and functions.




Functional levels

◆ Register transfer level

- Referring to the ability to describe the circuit as data assignment.

◆ Behavioral level

 - Referring to the ability to describe the behavior of circuit using abstract constructs such as loops and processes.



Levels of modeling

Analog-transistor level

- Uses an electronic model of circuit elements such as resistor, capacitor, and inductor.
- Allows analog values of voltages or currents to represent logic values on the interconnections.

Switch level

- Describes the interconnection of transmission gates which are abstractions of individual MOS and CMOS transistors.

Logic level

- Describes a digital circuit in terms of primitive logic functions such as AND, OR, NAND, and NOR.
- Allows for the nets interconnecting the logic functions to carry 0, 1, x, and z.

Built-in gates and switches


n_input gates	n_output gates	three-state gates	pull gates	MOS switches	bidirectional switches
and	buf	bufif0	pulldown	cmos	rtran
nand	not	bufif1	pullup	nmos	rtranif0
nor		notif0		pmos	rtranif1
or		notif1		rcmos	tran
xnor				rnmos	tranif0
xor				rpmos	tranif1

Variable input/output logic gates

❏ The gates (and, nand, nor, or, xor, xnor) shall have one output and one or more inputs.

◆ The first terminal shall be output.

 and Uand (out, in1, in2);
or Uor (out, in1, in2, in3);



and	0	1	x	z
0	0	0	0	0
1	0	1	x	x
x	0	x	x	x
z	0	x	x	x

nand	0	1	x	z
0	1	1	1	1
1	1	0	x	x
x	1	x	x	x
z	1	x	x	x

or	0	1	x	z
0	0	1	x	x
1	1	1	1	1
x	x	1	x	x
z	x	1	x	x

nor	0	1	x	z
0	1	0	x	x
1	0	0	0	0
x	x	0	x	x
z	x	0	x	x

xor	0	1	x	z
0	0	1	x	x
1	1	0	x	x
x	x	x	x	x
z	x	x	x	x

xnor	0	1	x	z
0	1	0	x	x
1	0	1	x	x
x	x	x	x	x
z	x	x	x	x

Buffers

Multiple output logic gates

- ♦ buf: simply bypass
- ♦ not: inverter

```
buf Ubuf (out1, in);
buf Ubuf (out1, out2, in);
```




buf		not	
input	output	input	output
0	0	0	1
1	1	1	0
x	x	x	x
z	x	z	x

Tri-state buffers

Tri-state buffer gates

- ♦ bufif0: buffer with active low control
- ♦ bufif1: buffer with active high control
- ♦ notif1: inverter buffer with active high control
- ♦ notif0: inverter buffer with active low control

```
bufif1 Ubf1 (out, in, control);
```

 

bufif0	CONTROL				
		0	1	x	z
D	0	0	z	L	L
A	1	1	z	H	H
T	x	x	z	x	x
A	z	x	z	x	x

bufif1	CONTROL				
		0	1	x	z
D	0	z	0	L	L
A	1	z	1	H	H
T	x	z	x	x	x
A	z	z	x	x	x

notif0	CONTROL				
		0	1	x	z
D	0	1	z	H	H
A	1	0	z	L	L
T	x	x	z	x	x
A	z	x	z	x	x

notif1	CONTROL				
		0	1	x	z
D	0	z	1	H	H
A	1	z	0	L	L
T	x	z	x	x	x
A	z	z	x	x	x

MOS switches

- MOS switches are unidirectional channels for data similar to the buff gates.


- Normal MOS

- pmos
 - nmos
 - cmos

- Resistive MOS

- It has significantly higher impedances between sources and drains when it conduct than pmos/nmos.
 - rpmos
 - rnmos
 - rcmos
 
```
pmos Up (out, data, control);
nmos Un (out, data, control);
cmos Uc (out, data, ncon, pcon);
```



pmos rpmos	CONTROL				
		0	1	x	z
D	0	0	z	L	L
A	1	1	z	H	H
T	x	x	z	x	x
A	z	z	z	z	z

nmos rnmos	CONTROL				
		0	1	x	z
D	0	z	0	L	L
A	1	z	1	H	H
T	x	z	x	x	x
A	z	z	z	z	z

Copyright © 2014 by Ando Ki

Introduction to Verilog-HDL module (9)

Bidirectional pass switch

- Bidirectional pass switch

- tran, rtan
 - tranif1, rtranif1
 - tranif0, rtranif0

- These pass switch shall not delay signals propagating through them.

- However, these can have turn-on and turn-off delays.

```
tran (inout1, inout2);
tranif1 (inout1, inout2, control);
```



Copyright © 2014 by Ando Ki

Introduction to Verilog-HDL module (10)

Pullup and pulldown sources


- A pullup source shall place a logic value 1 on the nets connected in its terminal list.
- A pulldown source shall place a logic value 0 on the nets connected in its terminal list.
  
```
pullup Up1 (net1);
pulldown Ud1 (net2);
```



Gate delay

- The gate delay specification can be zero, one, two, or three delays.
 - ◆ If there is no delay specification, there shall be no propagation delay through the gate.
 - 'and Uand(out, in1, in2);'
 - ◆ If there is one delay specification, it shall apply to both the rise and fall delay.
 - 'and #(3) Uand(out, in1, in2);'
 - ◆ If there are two delays, the first specifies rise delay and the second specifies fall delay.
 - 'and #(3, 5) Uand(out, in1, in2);'
 - ◆ If there are three delays, the last one is for turn-off delay.
 - Logic gates do not have the third delay.
 - Buffer gates can have this.
- #(1st delay[, 2nd delay[, 3rd delay]])
 - ◆ The first delay: rise delay
 - ◆ The second delay: fall delay
 - ◆ The third delay: turn-off delay
 - The transition to the high-impedances value.
- Each delay can be min:typ:max values
 - ◆ 'and #(1:2:3,2:1:3) U(y, x, z);'

 

Gate instantiation

```
GateType [strength] [delay] ListOfGateInstances;
```

```
and UA (out, in1, in2);  
and UB (out1, in1, in2);
```

```
and UC (out1, in1, in2), UD (out2, in1, in2);
```

Note comma
separation

```
and (out3, in1, in2, in3), (out4, in1, in2);
```

Note there are no
instance name.

❏ 'GateType' is one of 'and, or, ..., buf, ...'.

❏ 'ListOfGateInstances' is a comma-separated list which specifies the terminals of each gate and optionally names each instance.

❏ 'delay' will be #(r, f, t) form, where rise, fall, and transition (or turn-off).


❏ 'strength' specifies strength of driving, such as supply, strong, pull, and weak.

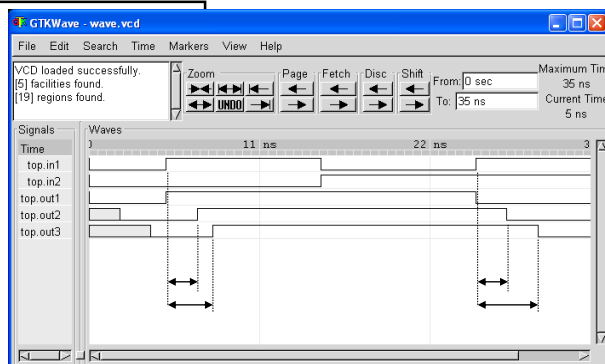Example of gate delay (1/2)



❏ 'codes/verilog/gate_switch/gate_delay'


```
`timescale 1ns/1ns  
module top;  
  reg in1, in2;  
  wire out1, out2, out3;  
  xor UxorA (out1, in1, in2);  
  xor #(2) UxorB (out2, in1, in2);  
  xor #(3, 4) UxorC (out3, in1, in2);  
  initial begin  
    in1 = 0; in2 = 0; #5;  
    in1 = 1; in2 = 0; #10;  
    in1 = 0; in2 = 1; #10;  
    in1 = 1; in2 = 1; #10;  
    in1 = 0; in2 = 0; #5;  
    $finish;  
  end  
end  
initial begin  
  $dumpfile("wave.vcd");  
  $dumpvars(1, in1, in2, out1, out2, out3);  
end  
endmodule
```



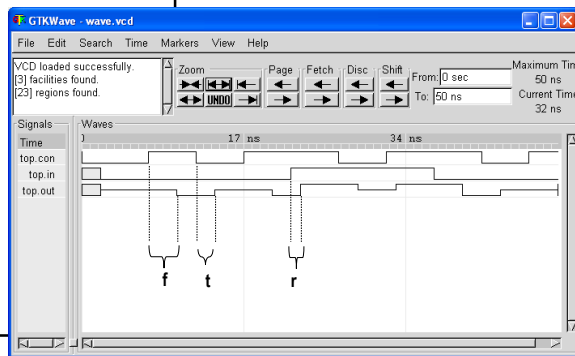Example of gate delay (2/2)

'codes/verilog/gate_switch/buf_delay'

```
`timescale 1ns/1ns
module top;
  reg in, con;
  wire out;
  bufif1 #(1, 3, 2) Ub (out, in, con); // r, f, t
  initial begin
    con = 0; #2;
    in = 0; #5; con = 1; #5; con = 0; #5; con = 1; #5;
    in = 1; #5; con = 0; #5; con = 1; #5;
    in = 0; #5; con = 0; #5; con = 1; #5;
    $finish;
  end
  initial begin
    $dumpfile("wave.vcd");
    $dumpvars(1, in, out, con);
  end
endmodule
```



Copyright © 2014 by Ando Ki

Introduction to Verilog-HDL module (15)

Example of gate-level model



'codes/verilog/gate_switch/dff_gate'

•Guess what will happen if the NAND gates have no delay.



```
`timescale 1ns/1ns
module top;
  reg d, clk;
  wire q, qb;
  initial begin
    clk = 0; forever #5 clk = ~clk;
  end
  initial begin
    d = 0; #7; d = 1; #10;
    d = 0; #10; d = 1; #10;
    d = 0; #10;
    $finish;
  end
  dff Udff (q, qb, d, clk);
endmodule

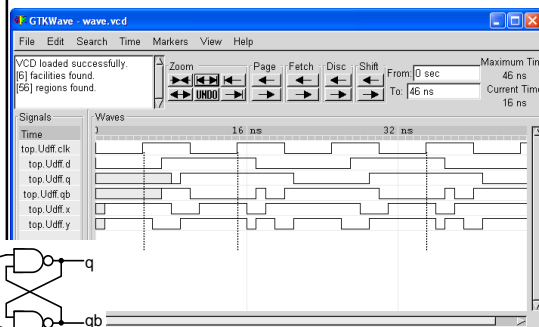 module dff (q, qb, d, clk);
  output q, qb;
  input d, clk;
  wire x, y;
  nand #1 U1 (q, x, qb); nand #1 U2 (qb, q, y);
  nand #1 U3 (x, d, clk); nand #1 U4 (y, x, clk);
  initial begin
    $dumpfile("wave.vcd");
    $dumpvars(1, clk, d, q, qb);
    $dumpvars(1, x, y);
  end
endmodule
```



Copyright © 2014 by Ando Ki

Introduction to Verilog-HDL module (16)


Example of switching-level model

```
`timescale 1ns/1ns


module top;
  reg in;
  wire out;
  inverter Uinv (out, in);
```

```
  initial begin
    in = 0; #10;
    in = 1; #15;
    in = 0; #20;
    in = 1; #5;
    $finish;
  end
  initial begin
    $dumpfile("wave.vcd");
    $dumpvars(1, out, in);
  end
endmodule
```
 
```
module inverter (out, in);
  output out;
  input in;
  //-----
  supply1 vdd;
  supply0 gnd;
  //-----
  pmos Upmos (out, vdd, in);
  nmos Unmos (out, gnd, in);
endmodule
```



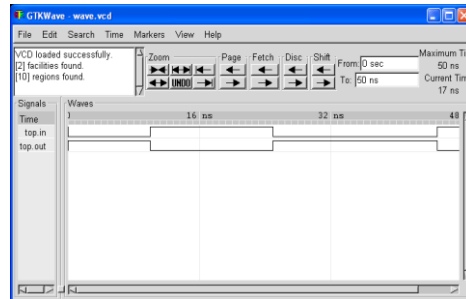'codes/verilog/gate_switch/inverter_switch'



Copyright © 2014 by Ando Ki


Introduction to Verilog-HDL module (17)

Example of pullup/pulldown (1/2)


```
`timescale 1ns/1ns
```

```
module top;
  ...
endmodule
```
 
```
module inverter (out, in);
  output out;
  input in;
  //-----
  supply1 vdd;
  supply0 gnd;
  //-----
  pmos #(1) Upmos (out, vdd, in);
  nmos #(3) Unmos (out, gnd, in);
  //-----
  pullup pu (out);
  pulldown pd (out);
endmodule
```



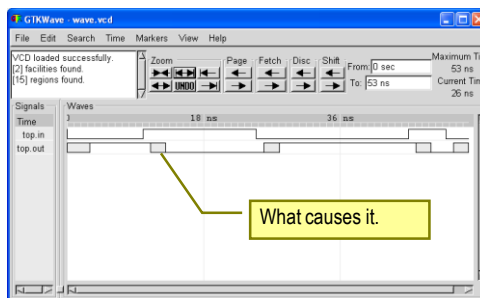'codes/verilog/gate_switch/inverter_pull'



Copyright © 2014 by Ando Ki


Introduction to Verilog-HDL module (18)

Example of pullup/pulldown (2/2)


```

`timescale 1ns/1ns
module top;
  reg data, cont;
  tri resultA, resultB;
  tri resultPA, resultPB;
  // without pull-up/down
  bufif1 Ua (resultA, data, cont);
  notif0 Ub (resultB, data, cont);
  // with pull-up/down
  bufif1 Upa (resultPA, data, cont);
  notif0 Upb (resultPB, data, cont);
  pulldown (resultPA);
  pullup (resultPB);
  initial begin
    data = 0;
    cont = 0;
    #5 cont = 1;
    #5 cont = 0;
    #5 data = 1;
    #5 cont = 1;
    #5 cont = 0;
    #5 $finish;
  end
  initial begin
    $dumpfile("wave.vcd");
    $dumpvars(1, data, cont, resultA, resultB);
    $dumpvars(1, resultPA, resultPB);
  end
endmodule

```

 

'codes/verilog/gate_switch/buf_pull'

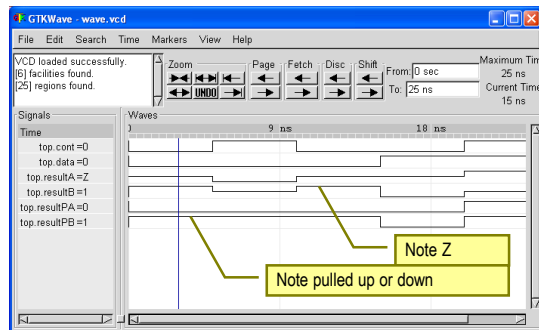

Copyright © 2014 by Ando Ki

Introduction to Verilog-HDL module (19)

Charge decay of trireg net

'treg #(rise, fall, charge_decay) instance;'

- ◆ No decay without charge_decay.
- ◆ After charge_decay time, the trireg net makes a transition from 1 or 0 to X.



'codes/verilog/gate_switch/charge_decay'



```

`timescale 1ns/1ns
module top;
  reg data, cont;
  trireg capA;
  trireg #(1,2,10) capB;
  nmos UA(capA, data, cont);
  nmos UB(capB, data, cont);
  initial begin
    data = 1; cont = 0; #5; cont = 1; #10;
    data = 0; cont = 0; #30; cont = 1; #10
    cont = 0; #30; cont = 1; #5
    #30 $finish;
  end
  initial begin
    $dumpfile("wave.vcd");
    $dumpvars(1, data, cont, capA, capB);
  end
endmodule

```

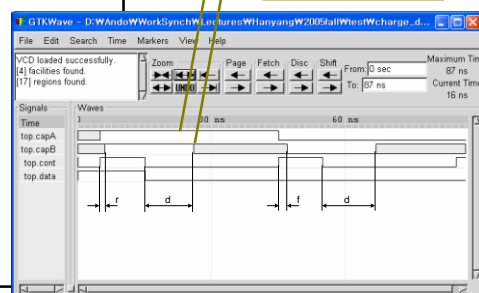 

Copyright © 2014 by Ando Ki

Introduction to Verilog-HDL module (20)

UDP

❏ User-defined primitive

- ◆ Independent module
- ◆ The same level as module definition
 - ❏ It can be appear anywhere in the source, either before or after it is instantiated inside a module.
 - ❏ It shall not be appear in module definition, i.e., between 'module' and 'endmodule'.
- ◆ Instances of new UDP's can be used in exactly the same manner as the gate primitives.
- ◆ Each UDP has exactly one output.
- ◆ Value of UDP output can be 0, 1, or X.
 - ❏ Z is not supported.
 - ❏ Z in input will be X in the UDP.

❏ Types of UDP

- ◆ Combinational UDP
 - ❏ Uses the value of its inputs to determine the next value of its output.
- ◆ Sequential UDP
 - ❏ Uses the value of its inputs and the current value of its output to determine the value of its output.

Form of UDP

❏ UDP has exactly one output port.

- ◆ The output port must come first in the comma-separated list of ports.

❏ UDP has none or multiple input ports.

❏ Bidirectional port is not permitted.

❏ All port shall be scalar.

- ◆ Vector ports are not permitted.

❏ Combinational UDP

- ◆ Cannot has 'reg'.

❏ Sequential UDP

- ◆ Can have 'reg' declaration for the output port.
- ◆ Can have 'initial' block.
 - ❏ It specifies the value of the output port when simulation begins.

```
primitive name_of_UDP (oport [, iport1 [, iport2 [, ...]]]);
output oport; [reg oport]
[input iport1; [input iport2; [input iport3; [...]]]]
[initial oport = initial_value;]
table
...
endtable
endprimitive
```

UDP table

The state table of UDP defines the behavior of a UDP.

Symbol	Interpretation	Comments
0	Logic 0	
1	Logic 1	
x	Unknown	Permitted in the input fields of all UDPs and in the current state field of sequential UDPs.
?	Iteration of 0, 1, and x	Not permitted in output field.
b	Iteration of 0 and 1	Permitted in the input fields of all UDPs and in the current state field of sequential UDPs. Not permitted in the output field.
-	No change	Permitted only in the output field of a sequential UDP.
(vw)	Value change from v to w	v and w can be any one of 0, 1, x, ?, or b, and are only permitted in the input field.
*	Same as (??)	Any value change on input.
r	Same as (01)	Rising edge on input.
f	Same as (10)	Falling edge on input.
p	Iteration of (01), (0 x) and (x1)	Potential positive edge on the input.
n	Iteration of (10), (1x) and (x0)	Potential negative edge on the input.

```
// UDP table for combinational UDP
// iport1 iport2 iport3 ... : oport;
table
<UDP table symbol list for input ports> : <output port value> ;
endtable
```


```
// UDP table for sequential UDP
// iport1 iport2 iport3 ... : current_oport : next_oport;
table
<UDP table symbol list for input ports> : <current_oport> : <next_oport> ;
endtable
```

Combinational UDP example



'codes/verilog/gate_switch/udp_mux'
 
```
primitive
multiplexer (mux, control, dataA, dataB);
output mux;
input control, dataA, dataB;
table
// control dataA dataB mux
01 0 : 1 ;
01 1 : 1 ;
01 x : 1 ;
00 0 : 0 ;
00 1 : 0 ;
00 x : 0 ;
10 1 : 1 ;
11 1 : 1 ;
1x 1 : 1 ;
10 0 : 0 ;
1x 0 : 0 ;
x0 0 : 0 ;
x1 1 : 1 ;
endtable
endprimitive
```




```
primitive
multiplexer (mux, control, dataA, dataB);
output mux;
input control, dataA, dataB;
table
// control dataA dataB mux
01?:1 ; // ? = 0 1 x
00?:0 ;
1?:1 ;
1?:0 ;
x00:0 ;
x11:1 ;
endtable
endprimitive
```

Output port comes first.

'?' is '0', '1', and 'x'.

 '0xx' and '1xx' are not specified. Thus this will make 'x' for its output when it happens.



Sequential UDP examples (1/2)

codes/verilog/gate_switch/udp_ff


```
// level-sensitive sequential UDP
primitive latch (q, clock, data);
output q; reg q;
input clock, data;
table// clock data qq+
01 : ? : 1 ;
00 : ? : 0 ;
1? : ? :- ; // - = no change
endtable
endprimitive
```

Note 'reg'.

'?' is '0', '1', and 'x'.

```
// edge-sensitive sequential UDP
primitive d_edge_ff (q, clock, data);
output q; reg q;
input clock, data;
table
// clock data qq+
(01) 0:?:0; // obtain output on rising edge of clock
(01) 1:?:1; // obtain output on rising edge of clock
(0?) 1:1:1; // obtain output on rising edge of clock
(0?) 0:0:0; // obtain output on rising edge of clock
(??) ??:?:-; // ignore negative edge of clock
? (??):?:-; // ignore data changes on steady clock
endtable
endprimitive
```

 (01) Rising edge.
(10) Falling edge.
(??) Any value change.



Copyright © 2014 by Ando Ki

Introduction to Verilog-HDL module (25)

Sequential UDP examples (2/2)

codes/verilog/gate_switch/udp_dff

```
primitive dff1 (q, clk, d);
input clk, d;
output q; reg q;
initial q = 'b1;
table
// clk dq+
r0:?:0;
r1:?:1;
f?:?:-;
?*:?:-;
endtable
endprimitive
```




Note 'initial'.

Stable signal of clock does not affect the output even input changes.

'*' is the same as (??), any value change.

```
module dff (q, qb, clk, d);
input clk, d;
output q, qb;
dff1 g1 (q, clk, d);
buf #3 g2 (q, q);
not #5 g3 (qb, q);
endmodule
```

See how to instantiate UDP.

   


Copyright © 2014 by Ando Ki

Introduction to Verilog-HDL module (26)

Project


UDP half-adder

 - ◆ Make a half-adder in UDP.
 - Its module name is 'half_adder_udp'.
 - Thus, code 'half_adder_udp'.
- ◆ Apply it to the following hierarchy.
 - 'full_adder', and
 - 'top'.



Switch-level half-adder

 - ◆ Make a half-adder in switch-level.
 - Draw switch-level circuit using nMOS, pMOS, or cMOS.
 - Its module name is 'half_adder_switch'.
 - Thus code 'half_adder_switch.v'.
- ◆ Apply it to the following hierarchy.
 - 'full_adder', and
 - 'top'.



Reading

- IEEE Std. 1364-2001, IEEE Standard Verilog Hardware Description Language. (Chapter 7. Gate and Switch Level Modeling; Chapter 8. User Defined Primitives)